
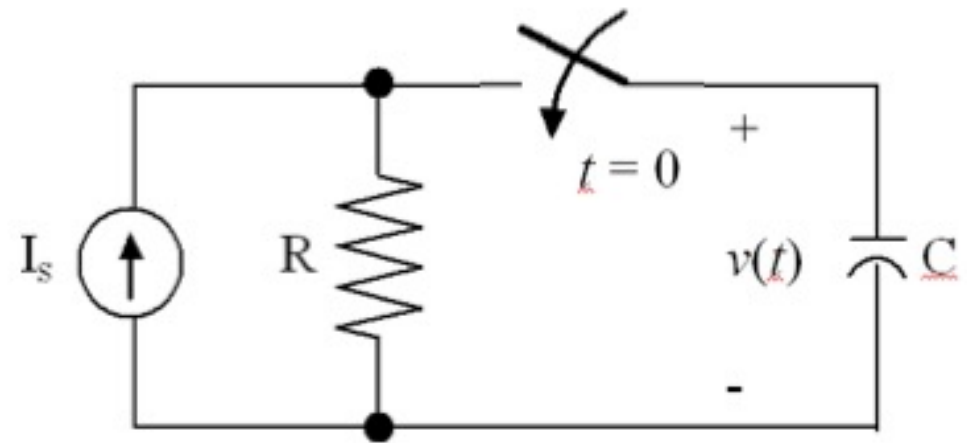


1st Order Transients – 2

general solution


First Order RC Case

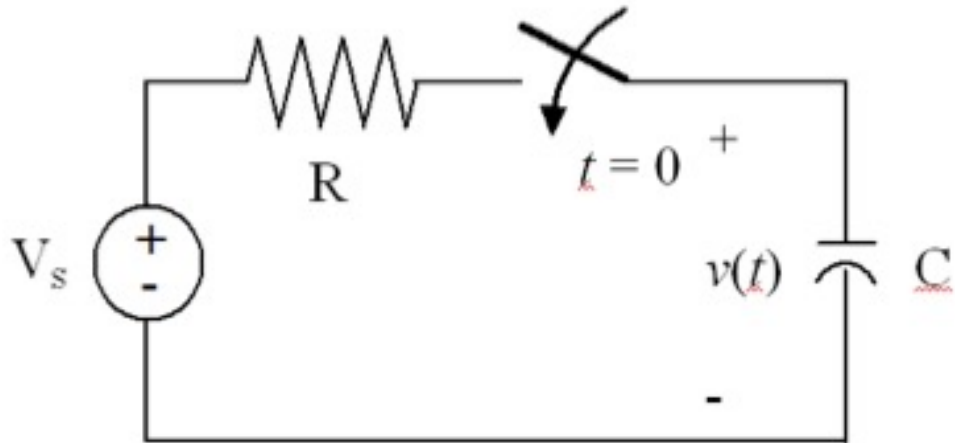

- Solution
$$v(t) = (v_0 - v_\infty) e^{-t/RC} + v_\infty$$

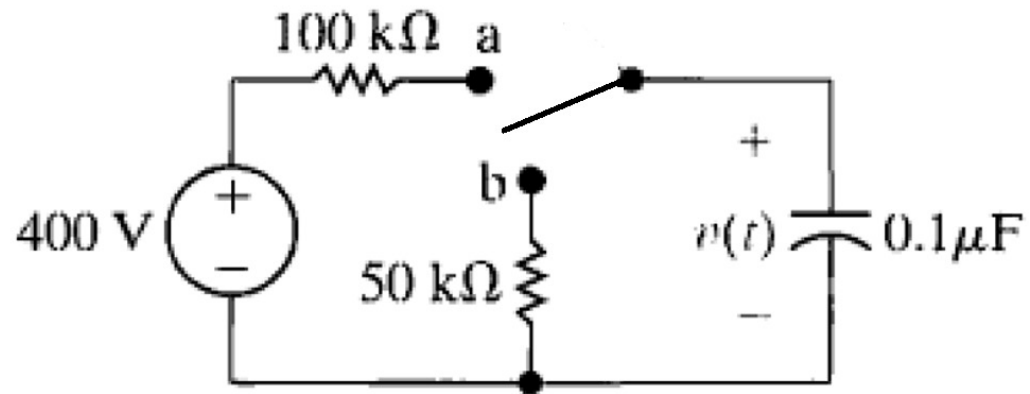
Example:

Switch changes $a \rightarrow b$ at $t = 0$





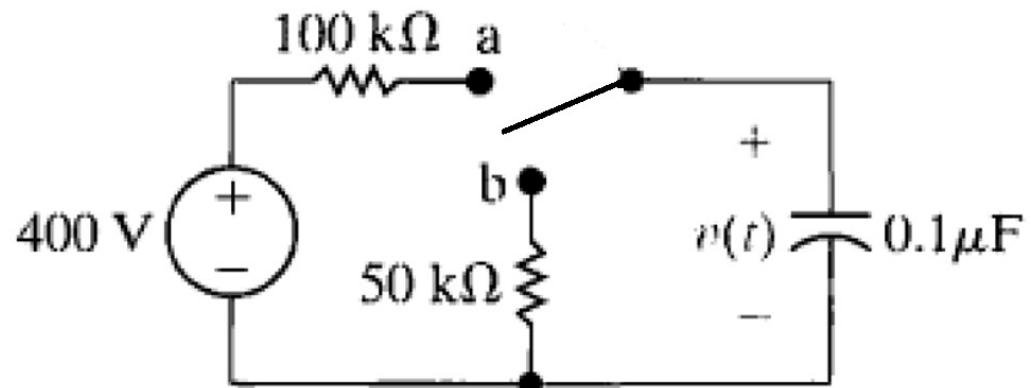Example:

Switch changes $b \rightarrow a$ at $t = 0$




First Order RL Case

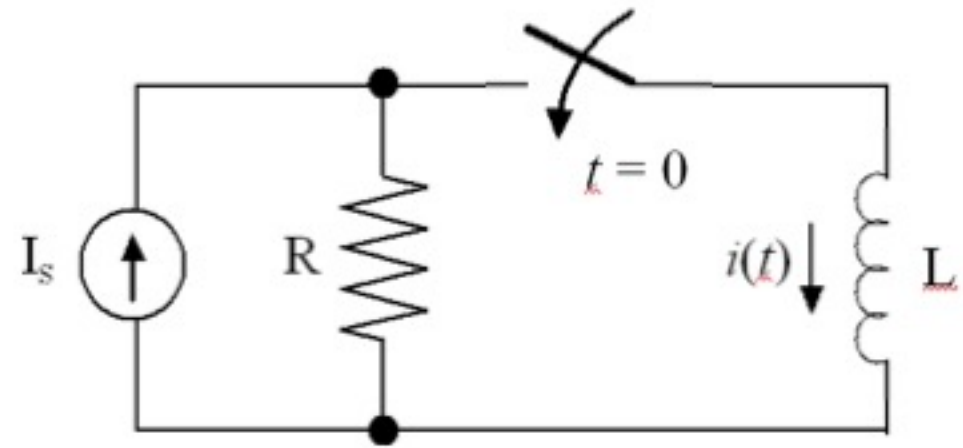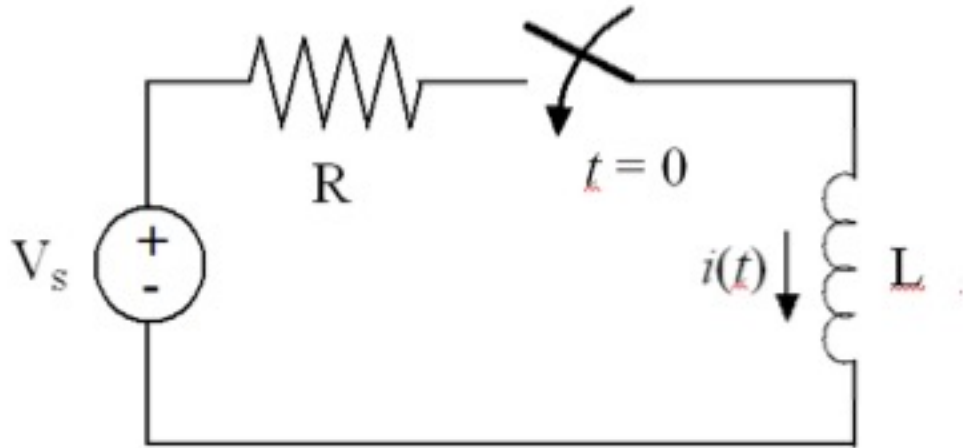

- Loop KVL equation:
$$\frac{di(t)}{dt} + \frac{R}{L} i(t) = \frac{1}{R} V_s$$
- Solution:
$$i(t) = (i_0 - i_\infty) e^{-\frac{R}{L}t} + i_\infty$$


Example:

Switch opens at $t = 0$

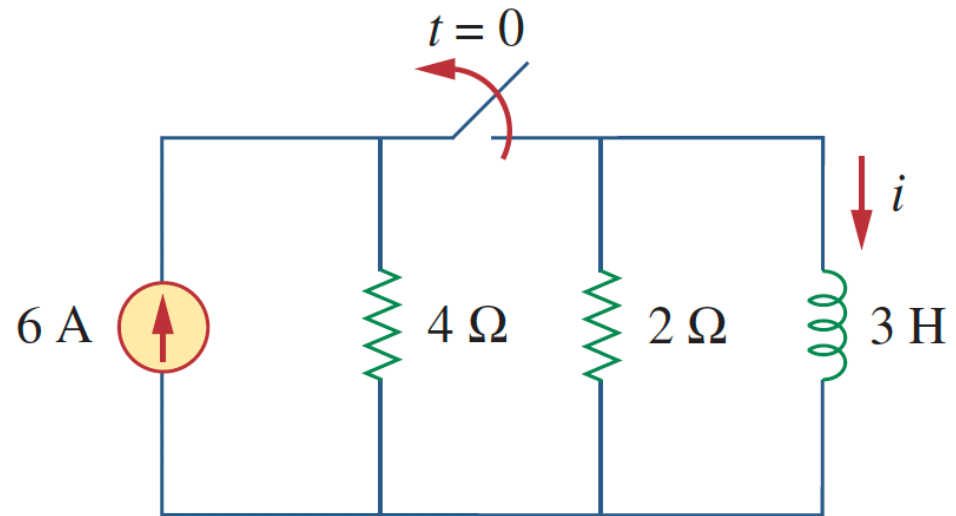

Example:

Switch closes at $t = 0$

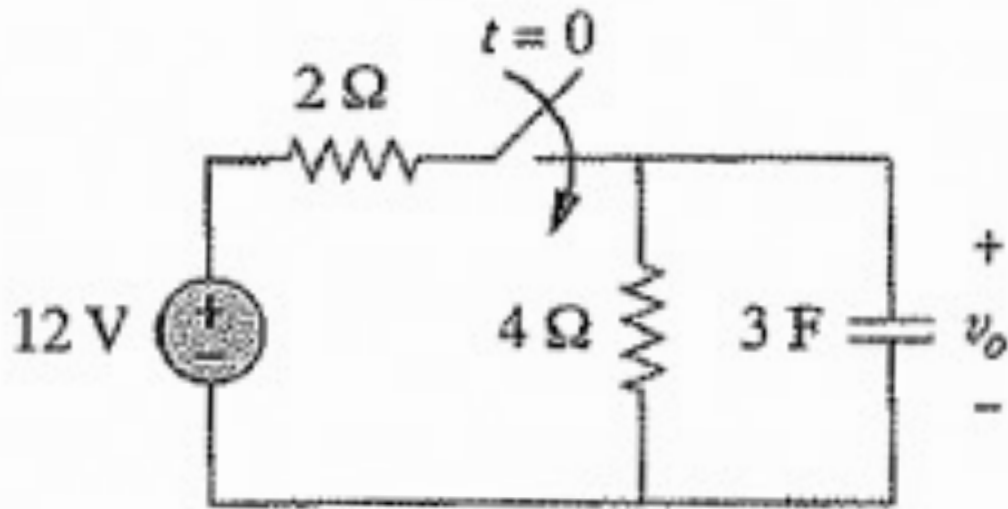

General Result – 1st Order

- Inductor current or capacitor voltage, $x(t)$ for $t > 0$


$$x(t) = [x(0) - x(\infty)] e^{-t/\tau} + x(\infty)$$

- Final and initial values, $x(\infty)$ and $x(0)$:
 - From a DC analysis based on “open” or “short” models for C and L
 - Initial value exploits the continuity of capacitor voltages and inductor currents at $t = 0$



$$x(t) = [x(0) - x(\infty)] e^{-t/\tau} + x(\infty)$$

- Time constant τ ($= L/R$ or RC)
- Why this form?
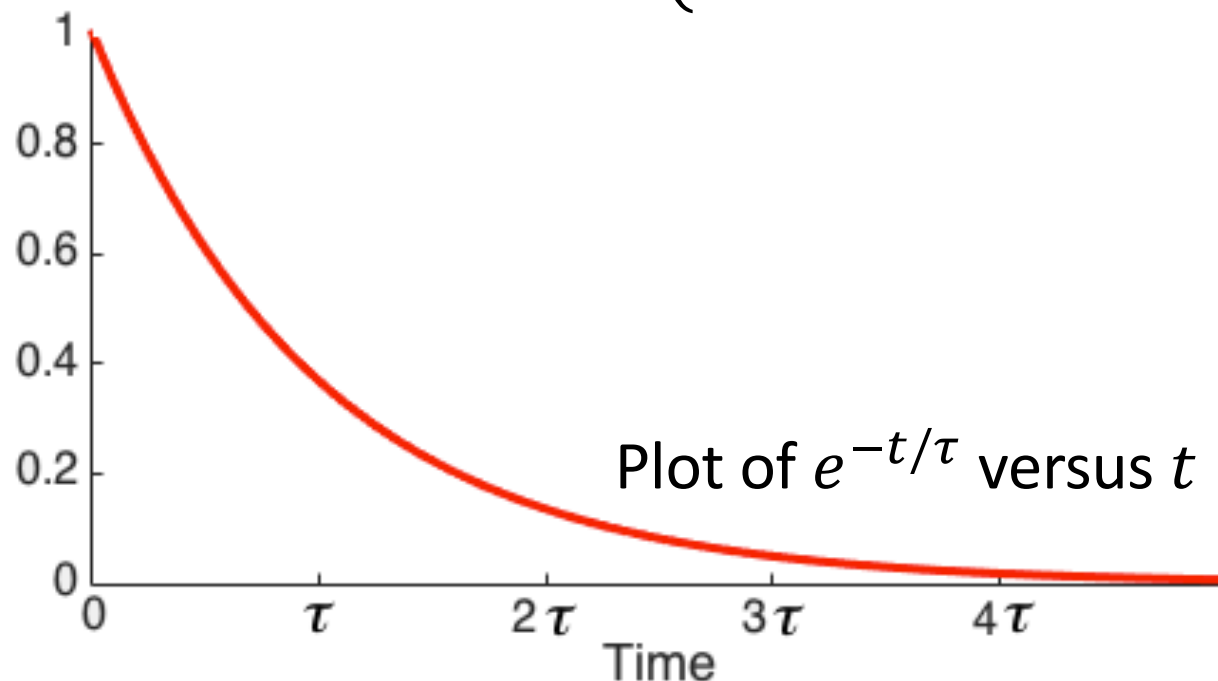
$$e^{-t/\tau} = \begin{cases} 1 & t = 0 \\ 0.369 & t = \tau \\ 0.002 & t = 4\tau \end{cases}$$




What if the Circuit is more Complex?

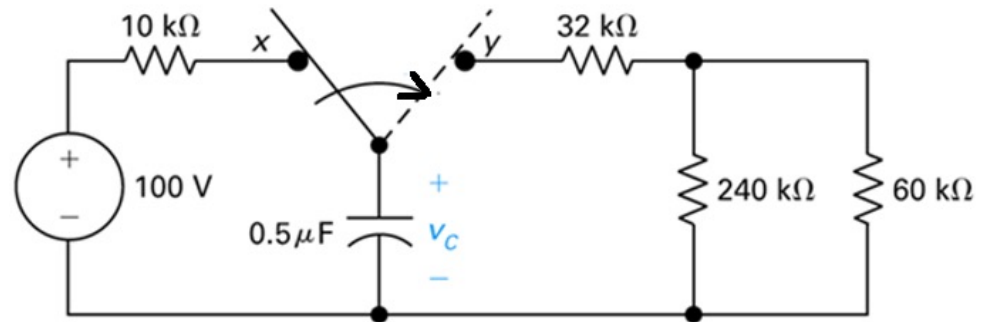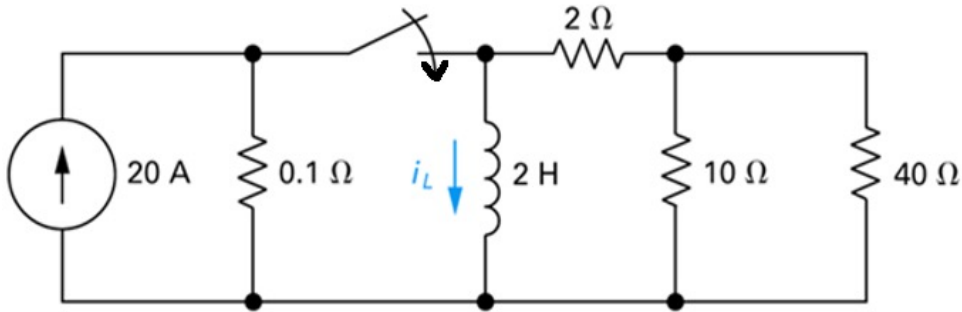

- Use the Thevenin equivalent circuit seen by L or C
 - Time constant $\tau = L/R_{Th}$ or $R_{Th}C$

Worked Example


- Find $i(t)$

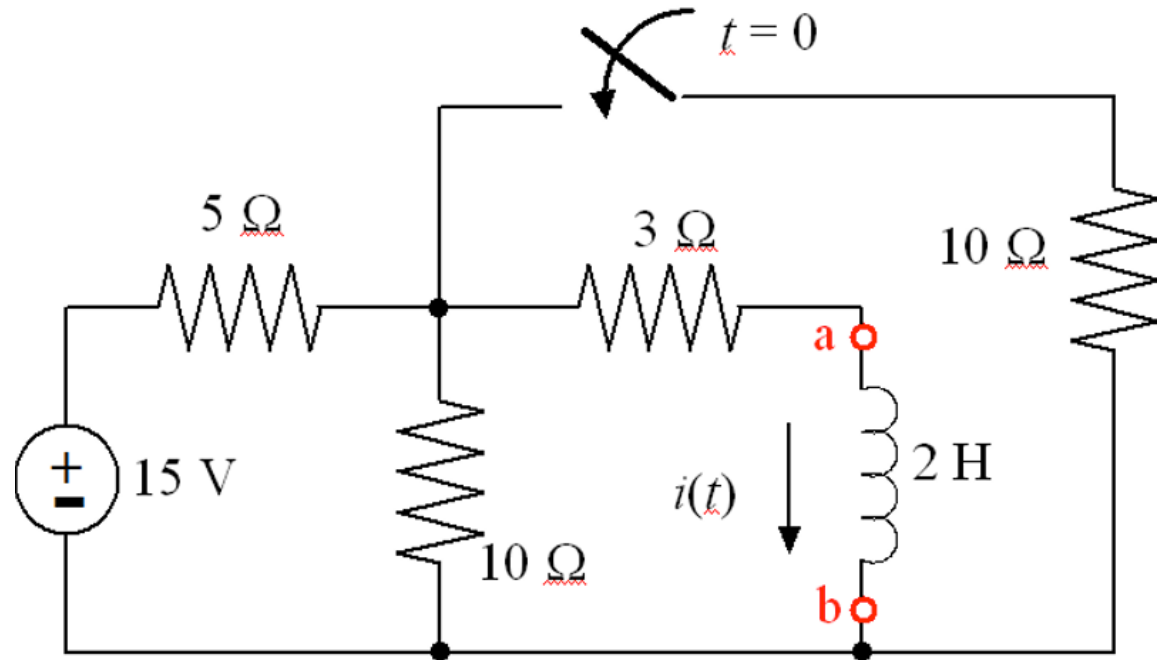

$$i(t) = (i_0 - i_\infty) e^{-t/\tau} + i_\infty$$

- Need: τ , i_∞ , and i_0

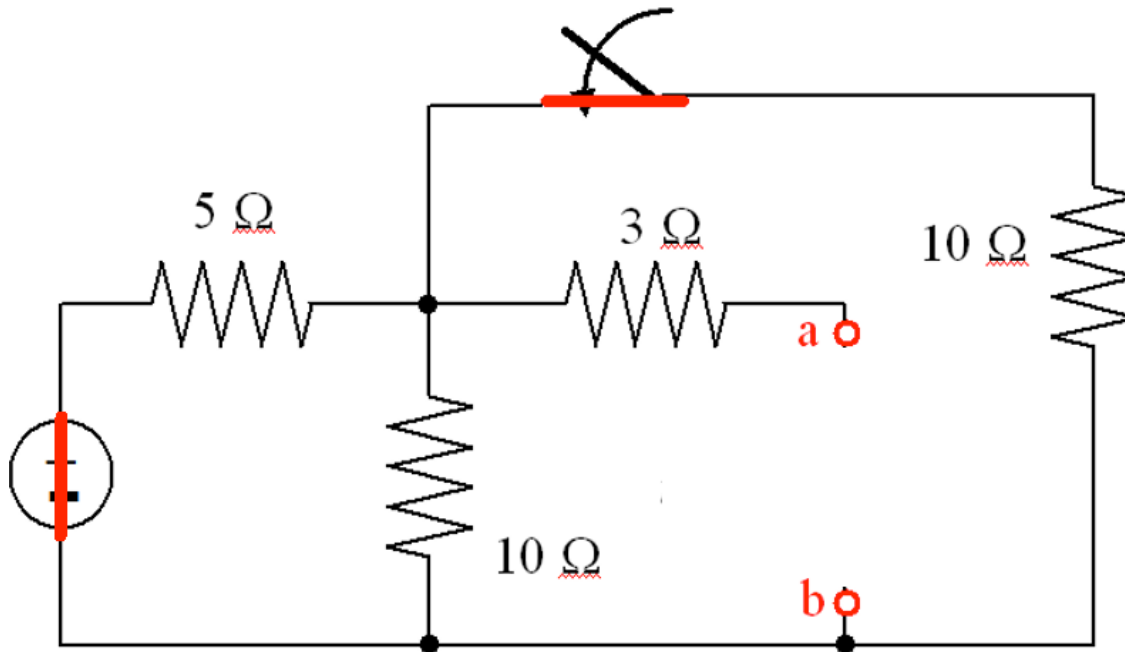
Step 1 – time constant $\tau = \frac{L}{R_{Th}}$



$$\begin{aligned} R_{Th} &= 3 + 5 || 10 || 10 \\ &= 3 + 5 || 5 \\ &= 5.5\ \Omega \end{aligned}$$

$$\tau = \frac{2}{5.5} = \frac{1}{2.75}\ \text{sec}$$

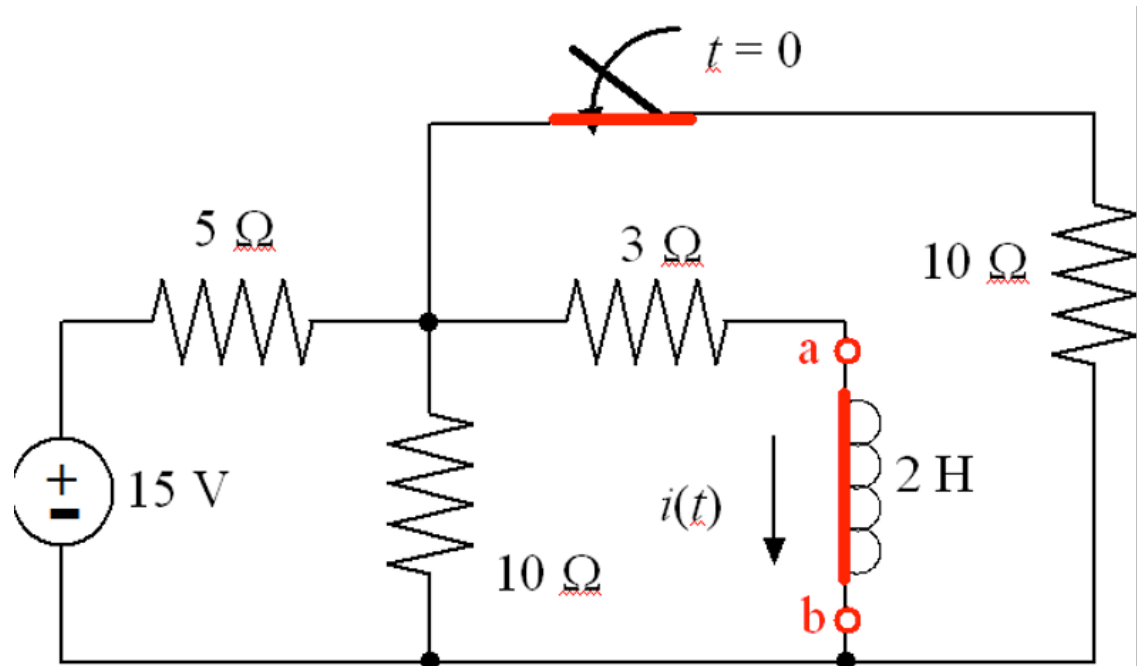
Step 2 – final value i_{∞} ; as $t \rightarrow \infty$



$$\frac{v - 15}{5} + \frac{v}{10} + \frac{v}{3} + \frac{v}{10} = 0 \Rightarrow v = \frac{45}{11}$$

$$i_{\infty} = \frac{v}{3} = \frac{15}{11} = 1.36 \text{ amps}$$


Step 3 – initial value i_0

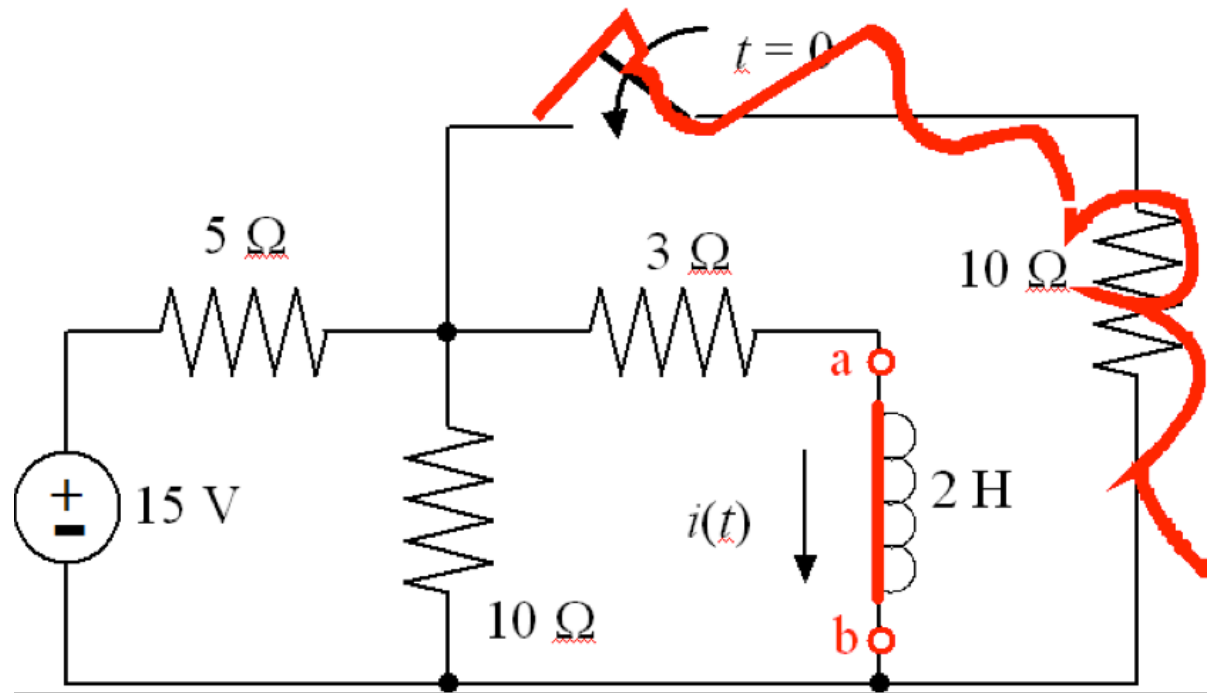


$$\frac{v - 15}{5} + \frac{v}{10} + \frac{v}{3} = 0 \Rightarrow v = \frac{90}{19}$$

$$i_0 = \frac{v}{3} = \frac{30}{19} = 1.58 \text{ amps}$$

Combining

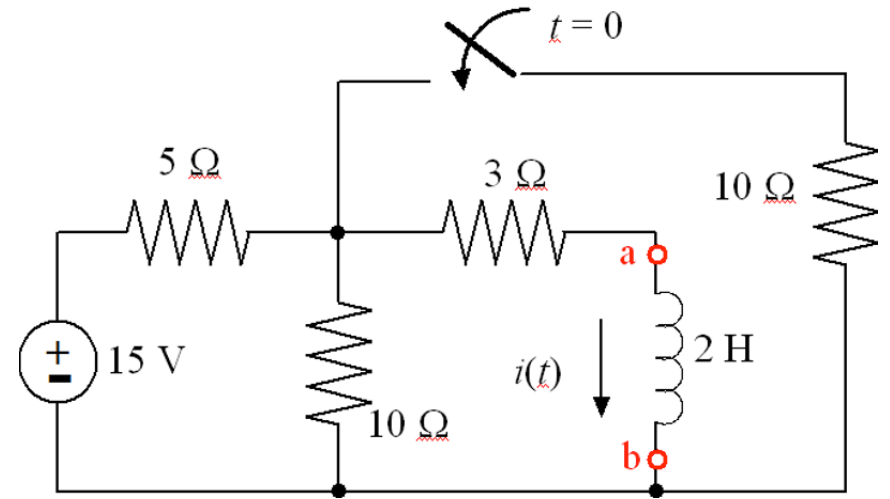

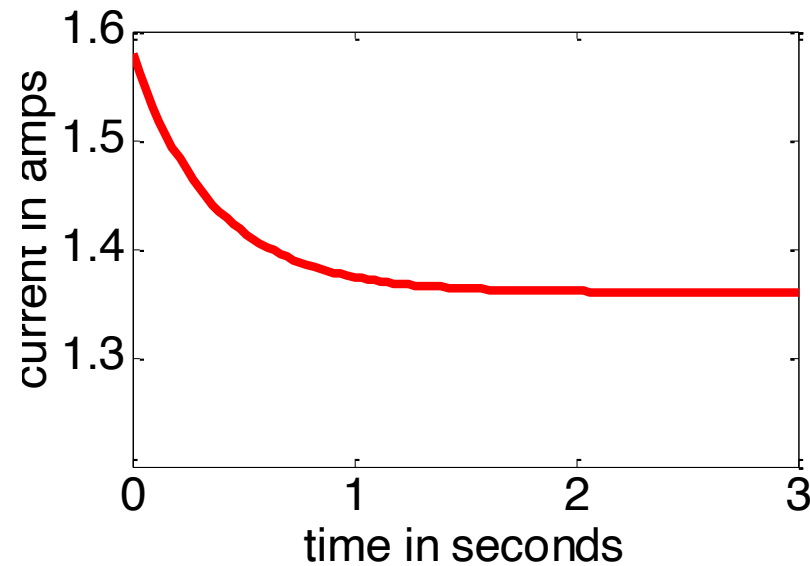
$$i(t) = (i_0 - i_\infty) e^{-2.75 t} + i_\infty$$
$$= 0.22 e^{-2.75 t} + 1.36 \text{ amps}$$



Practice Problem:


Find $i_L(t)$

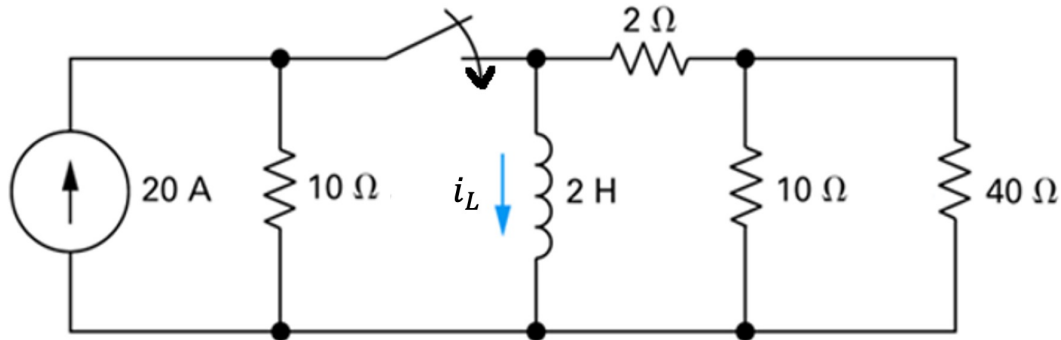

$$20 - 20e^{-2.5t} \text{ A}$$

Practice Problem:

Find $v_c(t)$

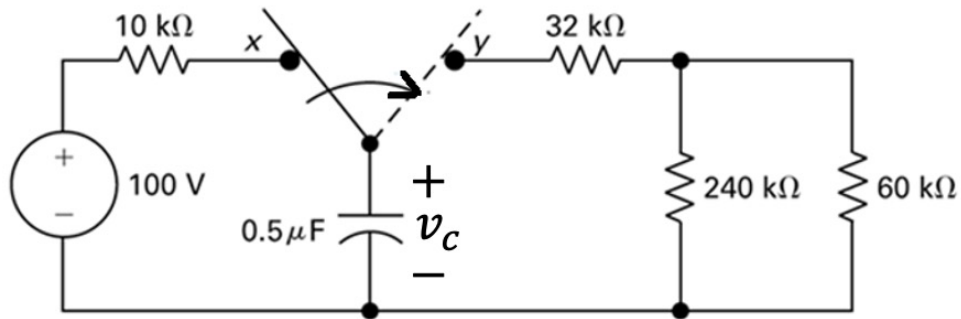

$$100 e^{-25 t} \text{ V}$$